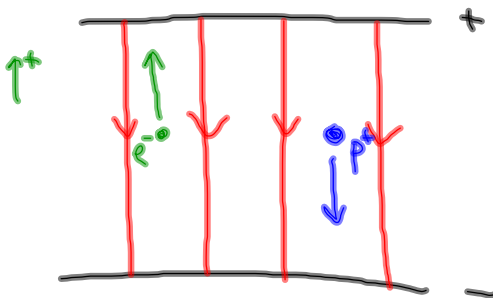


## Circuit Notes 1st Block 11.10.11

An electron and a proton are each placed at rest in an external uniform electric field of magnitude 520 N/C. Calculate the speed of each particle after 48 ns.

\* ignore gravity



$$e^- : v_f = v_i + a t$$

$$\Sigma \vec{F} = m_e \vec{a}$$

$$v_f = \frac{Eq_e t}{m_e}$$

$$a = \frac{\Sigma F}{m_e}$$

$$= \frac{F_e \text{ (electric force)}}{m_e}$$

$$\vec{E} = \frac{\vec{F}_e}{q} \quad \left. \begin{array}{l} \vec{F}_e = E q_e \\ \vec{F}_e = E q \end{array} \right\} = \frac{Eq_e}{m_e}$$

$$v_f = \frac{(520 \text{ N/C})(1.6 \times 10^{-19} \text{ C})(48 \times 10^{-9} \text{ s})}{(9.109 \times 10^{-31} \text{ kg})}$$

$$= 4.38 \times 10^6 \text{ m/s}$$


$$p^+ : v_f = \frac{Eq_p t}{m_p}$$

$$= \frac{(520 \text{ N/C})(1.6 \times 10^{-19} \text{ C})(48 \times 10^{-9} \text{ s})}{(1.673 \times 10^{-27} \text{ kg})}$$

$$= 2387 \text{ m/s}$$
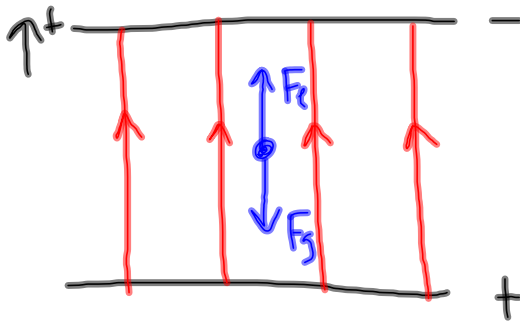
## Circuit Notes 1st Block 11.10.11

An object with a net charge of 24 microC is placed in a uniform electric field of 610 N/C, directed vertically. What is the mass of this object if it floats in this electric field?



$$q = 24 \mu\text{C}$$

$$E = 610 \text{ N/C}$$

$$m = ?$$

$$a_g = 9.8 \text{ m/s}^2$$

$$\Sigma \vec{F} = 0$$

$$F_e - F_g = 0$$

$$F_e = F_g$$

$$qE = ma_g$$

$$m = \frac{qE}{a_g}$$

$$= \frac{(24 \times 10^{-6} \text{ C})(610 \text{ N/C})}{(9.8 \text{ m/s}^2)}$$

$$= 1.49 \times 10^{-3} \text{ kg}$$

$$F_g = ma_g$$


$$F_e = qE$$

## Circuits:

### • Common Pieces:


<u>Piece</u>	<u>Schematic representation</u>
Wire	—
Battery	$\begin{array}{c} - \\   \\ + \end{array}$
Resistor	$\text{---}\text{---}\text{---}$
Capacitor	$\text{---}\text{---}$
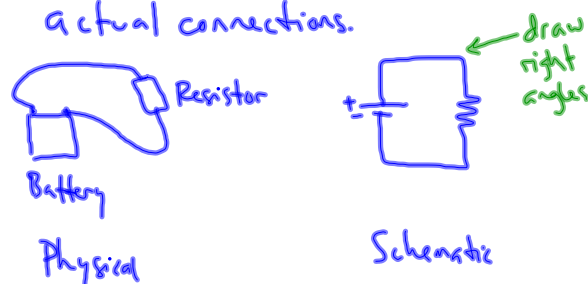
### • Schematic drawing to simulate the actual connections.



### • Ways to Connect Pieces:


#### 1. Series

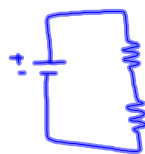

- pieces connected back-to-back
- $e^-$  only have one path to go on

- $e^-$  actually move from  $-$  to  $+$ .
- what we call current (conventional current) goes from  $+$  to  $-$ .

Series continued:

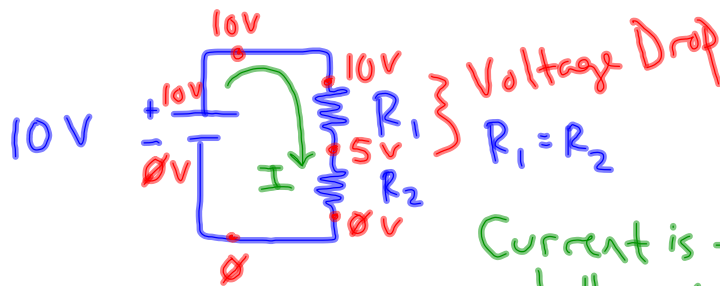

Current is the same in both resistors


\* More resistance means more voltage drop

- Ohm's Law:

$V = IR$  → resistance  
↳ voltage      ↳ current

Resistance units:  $1 \Omega = 1 \frac{V}{A}$   
(capital omega)

## 2. Parallel

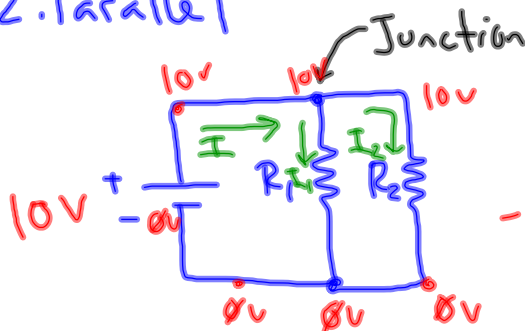

lines NOT connected

- Resistors have same voltage

- Current is different through resistors